

Summary in Graph

Exam Summary (GO Classes Test Series 2024 | Digital Logic | Test 2).

Qs. Attempted:	13 5 + 8	Correct Marks:	17 3 + 14
Correct Attempts:	10 3 + 7	Penalty Marks:	0 0 + 0
Incorrect Attempts:	3 2 + 1	Resultant Marks:	17 3 + 14

Total Questions:	15 5 + 10
Total Marks:	25 5 + 20
Exam Duration:	45 Minutes
Time Taken:	45 Minutes

- EXAM RESPONSE
- EXAM STATS
- FEEDBACK

Technical

Q #1


Numerical Type

Award: 1

Penalty: 0

Digital Logic

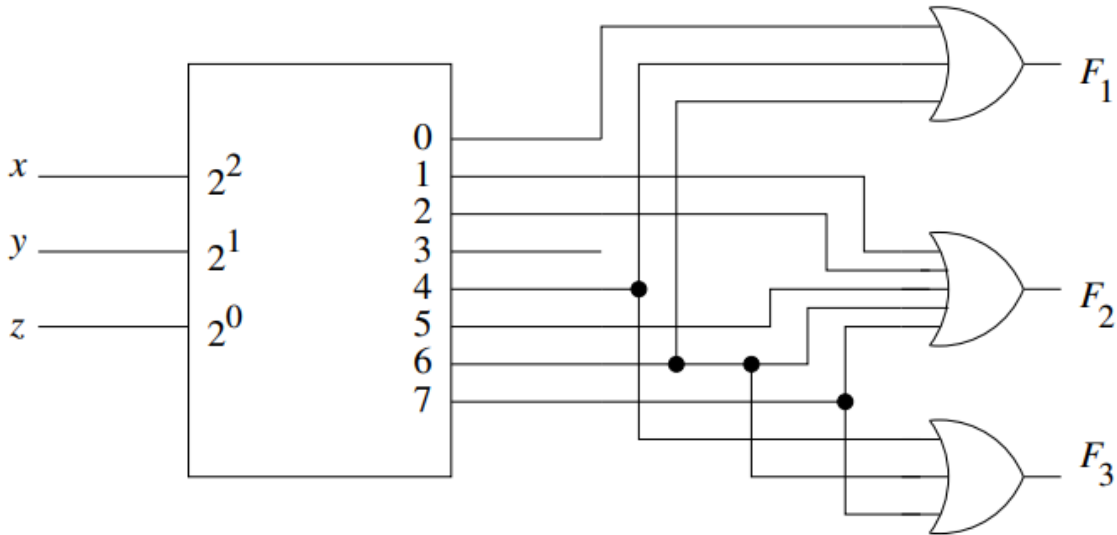Consider the following combinational circuit using a decoder and OR gates, implementing three Boolean functions  $F_1, F_2, F_3$  :



For how many input combinations  $(x, y, z)$ , at least two of these boolean functions are high?

Your Answer: 4

Correct Answer: 3

Incorrect

Discuss

Q #2

Numerical Type

Award: 1

Penalty: 0

Digital Logic

An  $8 \times 1$  multiplexer has inputs A, B and C connected to the selection inputs  $S_2$ (MSB),  $S_1$ , and  $S_0$ (LSB) respectively. The data inputs through  $I_0$  through  $I_7$  are as follows:

$$I_1 = I_2 = I_4 = 0; I_3 = I_5 = 1; I_0 = I_7 = D; \text{ and } I_6 = \overline{D}$$

Consider the Boolean function  $F(A, B, C, D)$  that this multiplexer implements. How many minterms of  $F$  are there for which  $F$  is 1?

Your Answer: 6

Correct Answer: 7

Incorrect

Discuss


Q #3

Multiple Choice Type

Award: 1

Penalty: 0.33

Digital Logic

 

- The figure above implements the Boolean function:
- A.  $F(x, y, z) = \Sigma(2, 3, 5, 6)$
  - B.  $F(x, y, z) = \Sigma(3, 4, 6, 7)$
  - C.  $F(x, y, z) = \Sigma(1, 3, 6, 7)$
  - D.  $F(x, y, z) = \Sigma(0, 2, 4, 6)$

Your Answer: B

Correct Answer: B

Correct

Discuss


Q #4

Multiple Choice Type

Award: 1

Penalty: 0.33

Digital Logic

 

The circuit above is to be used to implement the function  $z = f(A, B) = \overline{A} + B$ . Inputs I and J can be selected from the set  $\{0, 1, B, \overline{B}\}$ .

What values should be chosen for I and J?

- A.  $I = 0, J = B$
- B.  $I = 1, J = B$
- C.  $I = B, J = 1$

D.  $I = \overline{B}, J = 0$

Your Answer: B

Correct Answer: B

Correct

Discuss

Q #5

Multiple Choice Type

Award: 1

Penalty: 0.33

Digital Logic

Which of the following is the correct function for Full adder where inputs ' *a* ' and ' *b* ' are the numbers added, and input ' *c* ' is the carry-in. Also, ' *s* ' and ' *co* ' are sum and carry out, respectively.

- A.  $co = bc + ac + ab; s = a \text{ xor } b \text{ xor } c$
- B.  $co = b'c + a'c + ab; s = a \text{ xor } b \text{ xor } c$
- C.  $co = bc + ac + a'b'; s = a \text{ xor } b \text{ xor } c$
- D.  $co = bc + ac + ab; s = (ab) \text{ xor } c$

Your Answer: A

Correct Answer: A

Correct

Discuss

Q #6


Multiple Choice Type

Award: 2

Penalty: 0.67

Digital Logic

 As shown in the three diagrams below, device FA makes use of Two copies of device HA, and device D makes use of four copies of device FA. Assume that all basic logic gates(AND, OR, NOT, XOR gate) have the same delay *T*.



If all inputs to device D become available simultaneously, which output will be available last?

- A. *S*<sub>1</sub>
- B. *S*<sub>2</sub>
- C. *S*<sub>3</sub>
- D. They will all be available simultaneously.

Your Answer: C

Correct Answer: C

Correct

Discuss

Q #7


Numerical Type

Award: 2

Penalty: 0

Digital Logic

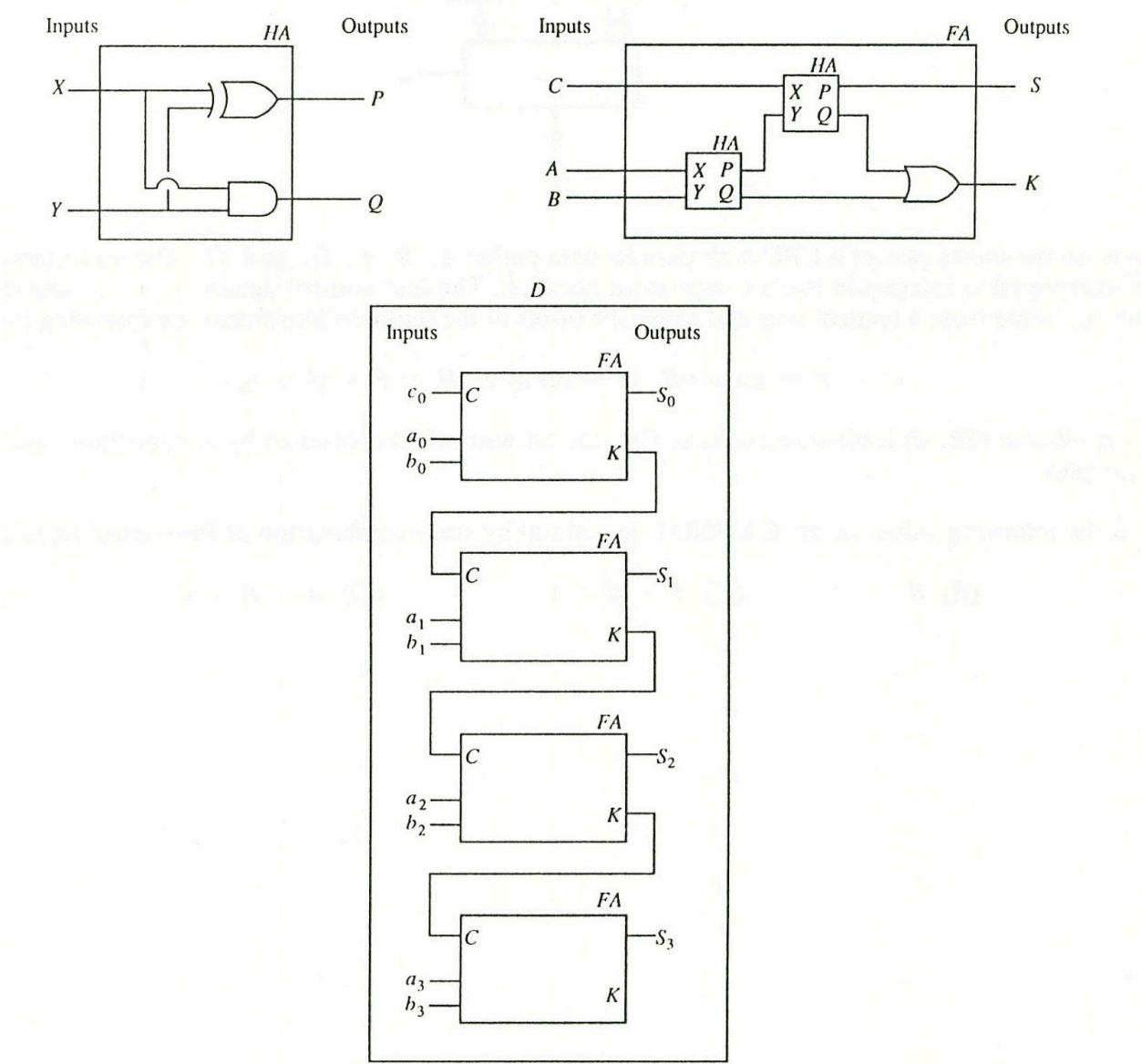As shown in the three diagrams below, device FA makes use of Two copies of device HA, and device D makes use of four copies of device FA. Assume that all basic logic gates(AND, OR, NOT, XOR gate) have the same delay  $T$ .



If all inputs to device D become available simultaneously, the delay before  $S_2$  must be valid is  $kT$ , then what is  $k$ ?

Your Answer: 8

Correct Answer: 6

Incorrect

Discuss


Q #8

Multiple Choice Type

Award: 2

Penalty: 0.67

Digital Logic

 

The logic circuit above is used to compare two unsigned 2-bit numbers,  $X_1X_0 = X$  and  $Y_1Y_0 = Y$ , where  $X_0$  and  $Y_0$  are the least significant bits. (A small circle on any line in a logic diagram indicates logical NOT.)


Which of the following always makes the output  $Z$  have the value 1?

- A.  $X > Y$
- B.  $X < Y$

 - C.  $X \neq Y$
- D.  $X \geq Y$

Your Answer: A    Correct Answer: A    Correct    Discuss

Q #9    Multiple Choice Type    Award: 2    Penalty: 0.67    Digital Logic




Above circuit represents

- A.  $2 \times 1$  MUX with A, B as input lines and C as a select line
- B.  $4 \times 1$  MUX with A, B as input lines and C as a select line
- C.  $2 \times 1$  MUX with A, C as input lines and B as a select line
- D.  $4 \times 1$  MUX with A, C as input lines and B as a select line

Your Answer: A    Correct Answer: A    Correct    Discuss

Q #10    Multiple Select Type    Award: 2    Penalty: 0    Digital Logic

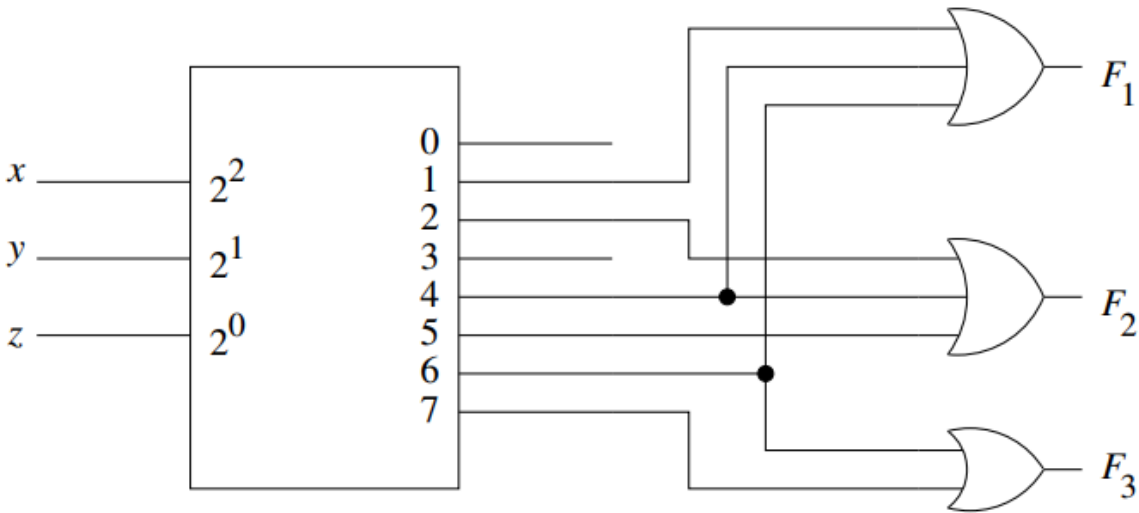Consider the following combinational circuit using a decoder and OR gates, implementing three Boolean functions  $F_1, F_2, F_3$  :




Which of the following is/are correct boolean expressions for these boolean functions?

- A.  $F_1 = x'y'z + xz'$
- B.  $F_2 = x'yz' + xy'$
- C.  $F_3 = xyz' + xz$
- D.  $F_3 = x'yz + xy$

Your Answer: A;B    Correct Answer: A;B    Correct    Discuss

Q #11    Multiple Choice Type    Award: 2    Penalty: 0.67    Digital Logic

 Consider the following combinational circuit:



By adding which term to this circuit, it will be free from "Static-1 Hazard"?

- A.  $XZ$
- B.  $XZ'$
- C.  $XY'Z + XYZ$
- D.  $XYZ$

Your Answer:

Correct Answer: A

Not Attempted

Discuss

Q #12

Multiple Choice Type

Award: 2

Penalty: 0.67

Digital Logic

We design a comparator circuit that takes two 4-bit words  $a_3a_2a_1a_0$  and  $b_3b_2b_1b_0$  as inputs, and generates one output  $f$  which is 1 iff the two words are identical, i.e.  $a_i = b_i$ , for all four bits ( $i = 0, 1, 2, 3$ ). Then which of the following is NOT a correct expression for  $f$ ?

- A.  $(a_3 \oplus b_3) + (a_2 \oplus b_2) + (a_1 \oplus b_1) + (a_0 \oplus b_0)$
- B.  $(a_3 \odot b_3) (a_2 \odot b_2) (a_1 \odot b_1) (a_0 \odot b_0)$
- C.  $(a_3 \odot b_3) + (a_2 \odot b_2) + (a_1 \odot b_1) + (a_0 \odot b_0)$
- D.  $(\overline{a_3} \oplus b_3) (\overline{a_2} \oplus b_2) (\overline{a_1} \oplus b_1) (\overline{a_0} \oplus b_0)$

Your Answer: C

Correct Answer: C

Correct

Discuss

Q #13


Multiple Choice Type

Award: 2

Penalty: 0.67

Digital Logic

 A multiplexer, shown below on the right, has 6 inputs,  $S_0, S_1, A, B, C$ , and  $D$ . The truth table on the left describes its function.



It is desired to implement the function  $F = (X \oplus Y) \oplus Z$  using the multiplexer. If  $X$  is applied to  $S_0$ , and  $Y$  is applied to  $S_1$ , what inputs should be applied to  $A, B, C$  and  $D$  to realize the function  $F$ ?

- A.  $A = B = C = D = Z$
- B.  $A = X \oplus Y, B = X \oplus Z, C = Y \oplus Z, D = Z$
- C.  $A = D = Z; B = C = \overline{Z}$
- D. the function  $F$  can not be realized with any of the inputs shown above.

Your Answer: C

Correct Answer: C

Correct

Discuss




Q #14

Multiple Choice Type

Award: 2

Penalty: 0.67

Digital Logic

 

The  $64K$  address space of a certain microcomputer is accessed by address signals  $A_0, A_1, \dots, A_{14}, A_{15}$  (Where  $A_0$  is the least significant bit and  $A_{15}$  is the most significant bit) and is divided equally among read-only memory(ROM), read-write memory(RAM), and input-output registers (I/O) by means of the decoder and gates as shown above.

Note that only the three high order outputs of the decoder are used. Output  $i(0 \leq i \leq 7)$  of the decoder is 1 if and only if the binary value of the inputs  $A_{15}A_{14}A_{13}$  is  $i$ .

Which of the following correctly indicates the beginning and ending hexadecimal addresses of the three portions of the address space?

- A. ROM (0000 - 3FFF), RAM ( 4000 - DFFF ), I/O ( E000 - FFFF )
- B. ROM (0000 - 9FFF), RAM ( A000 - DFFF ), I/O ( E000 - FFFF )
- C. ROM (A000 - DFFF), RAM ( 0000 - 9FFF ), I/O ( E000 - FFFF )
- D. ROM (4000 - 4FFF), RAM ( 6000 - FFFF ), I/O ( 0000 - 3FFF )

Your Answer: C

Correct Answer: C

Correct

Discuss


Q #15

Multiple Choice Type

Award: 2

Penalty: 0.67

Digital Logic

 

The figure above shows part of a CPU with parallel data paths  $A, B, F, G$  and  $H$ . The information on these paths is interpreted as integers in two's complement number notation. The four control signals  $x, y, z$ , and (the low-order carry-in)  $c_0$ , come from a control unit and cause the boxes in the figure to implement the following functions:

$$F = \overline{x}A \vee xB; G = yB \oplus z; H = F + G + c_0$$

Where  $\vee$  is bitwise *OR*,  $\oplus$  is bitwise exclusive *OR*, the bitwise AND is denoted by juxtaposition, and  $+$  is arithmetic plus.

Which of the following values of  $H$  CANNOT be realized by some combination of the control signals and  $c_0$ ?

- A.  $A$
- B.  $A + B + 1$
- C.  $A - B$
- D.  $A - B + 1$

Your Answer:

Correct Answer: D

Not Attempted

Discuss

You're doing good, you can target above 70 percentage!

[Copyright & Stuff](#)